



Electrical Engineering Department

Year: 2022 Semester: Fall 2022-2023

Course: EE – 321 / Electronic Circuits

Project Title:

Active Band Pass Filter (BPF) using Transistors

Due Date: 12/15/2022

Instructor: *Dr. Ahsan Rahman*

By

Marwan Bitar

4110259

Abstract

The transistors have many applications as we know. Therefore, I will build an active band pass filter using a special type of transistor. This type is an NPN-BJT. However, analysis, diagrams, calculations, and applications will be provided for the project. Finally, we can use this filter to tune some device to take specific frequencies and to have a creative idea in this project, we can add a potentiometer to have a variable band as well. So, it can be applied in various communication applications.

Content

1. Introduction	Page.2
2. Theory & Configuration	Page.2
3. Implementation & Analysis	Page.6
4. Conclusion	Page.10
5. References	Page.11

1. Introduction

One of the most important skills for an electrical engineer is designing and analyzing circuits. Electronics 2 course focuses on this particular objective in its project. As a result, in this report, I will design a BPF using NPN-BJT (NPN Bipolar Junction Transistor) that serves specific functions within a certain range. I will discuss the theory briefly, the configuration precisely, and the frequency response in details.

A bandpass filter (BPF) is a circuit that enables frequencies within a certain frequency range to pass through while rejecting (attenuating) frequencies outside that range. A bandpass filter usually is a combination between a low pass filter and a high pass filter. The constructed filter using transistor is an active filter. An active filter is a type of analog circuit implementing an electronic filter using active components, typically an **amplifier**. So, as we know, the constructing elements of the amplifiers are transistors of any type; BJTs, MOSFETs, JFETs, etc.

2. Theory & Configuration

❖ Theory

A BJT circuit is usually an active BPF circuit, so continuing with the idea that states that the BPF is combined form a LPS and a HPF, we will have two frequency responses for the BJT circuit.

These two responses are related to specific capacitors, and the following figure demonstrates this.

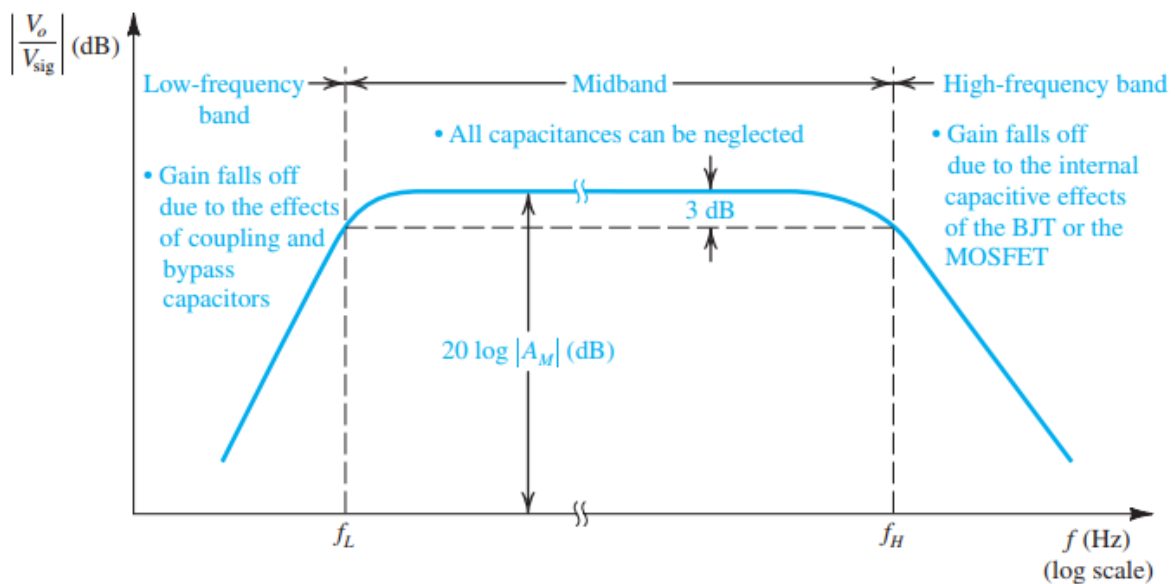


Figure 1 – Frequency responses due to capacitors

The main equation that is used to determine the frequency response is:

$$f = \frac{1}{2\pi RC}$$

Where:

f = the frequency in HZ.

R = the equivalent resistance related to the specific capacitor in Ω .

C = the capacitor that affects the frequency response in F.

And we can determine the bandwidth (or passband) by:

$$\text{bandwidth (BW)} = f_H - f_L$$

Where:

f_H = high band frequency in Hz.

f_L = low band frequency in Hz.

These frequencies depend on the type of the BJT circuit. So, I will discuss the low frequency response and the high frequency response equations in the Configuration subsection.

❖ Configuration

I will use a well-known NPN-BJT circuit called voltage divider common emitter configuration, and this circuit is shown in the following figure:

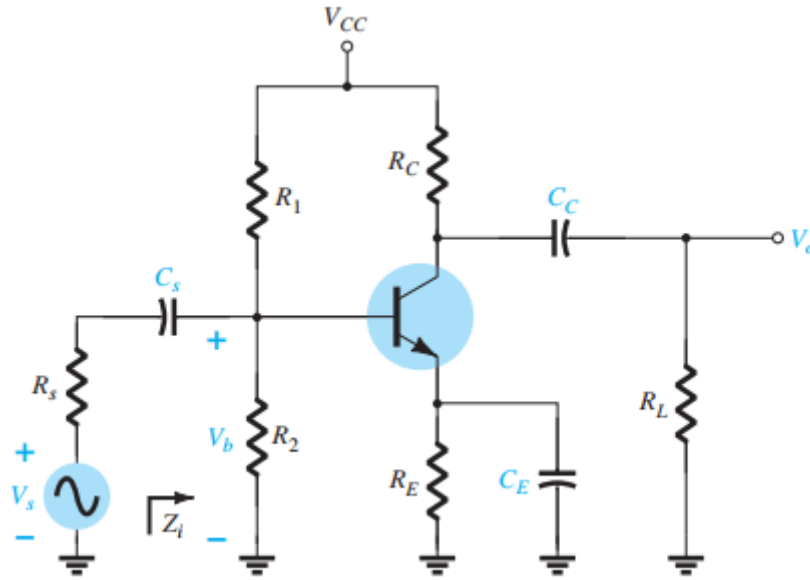


Figure 2 – Voltage divider common-emitter BJT circuit

The BJT circuit is an active BPF circuit, so continuing with the idea that states that the BPF is combined from a LPF and a high HPF, we can say that the BJT has two responses for each as mentioned. As a result, we will have two responses for this circuit:

- 1- Low Frequency Response: it is the greatest frequency response of a capacitor among the three bypassing and coupling capacitors (C_s , C_C , and C_E).
 $f_L = \max(f_s, f_C, f_E)$.

- a) Frequency response of (Capacitor S):

$$f_{L_s} = \frac{1}{2\pi(R_i + R_s)C_s} \quad R_i = R_1 \parallel R_2 \parallel \beta r_e$$

Where:

β = is the DC current gain (I_C/I_B).

r_e = The dynamic resistance of the BJT (internal resistance) in Ω .

- b) Frequency response of (Capacitor C):

$$f_{L_C} = \frac{1}{2\pi(R_o + R_L)C_C} \quad R_o = R_C \parallel r_o$$

Where:

r_o = The output resistance of the transistor in Ω .

c) Frequency response of (Capacitor E):

$$f_{L_E} = \frac{1}{2\pi R_e C_E} \quad R_e = R_E \parallel \left(\frac{R'_s}{\beta} + r_e \right) \text{ and } R'_s = R_s \parallel R_1 \parallel R_2$$

2- High Frequency Response: it is the smallest frequency response of a capacitor among the two output capacitances (C_i , C_o). $f_H = \min(f_{Hi}, f_{Ho})$.

We will have a new representation of our circuit as shown in the next figure:

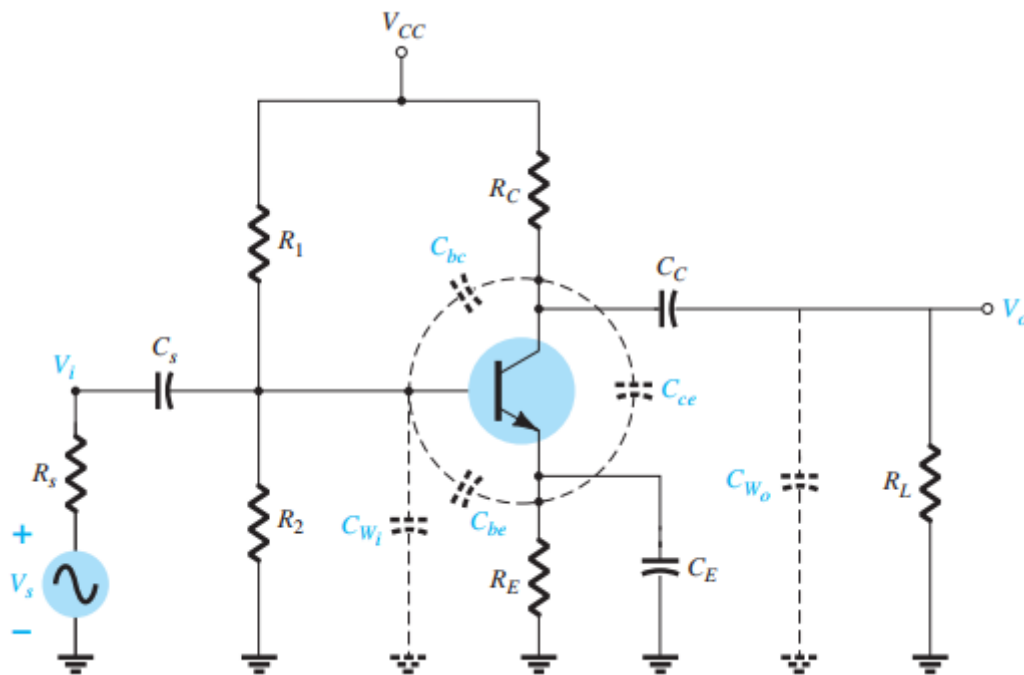


Figure 3 – Same BJT configuration with the effect of the output capacitance

i. Frequency response of C_i :

$$f_{H_i} = \frac{1}{2\pi R_{Th_i} C_i}$$

$$R_{Th_i} = R_s \parallel R_1 \parallel R_2 \parallel \beta r_e$$

$$C_i = C_{W_i} + C_{be} + C_{M_i} = C_{W_i} + C_{be} + (1 - A_v)C_{bc}$$

Where:

C_{W_i} = input wiring capacitance in F.

C_{be} = internal capacitance of the BJT from base to emitter in F.

C_{M_i} = input Miller effect capacitance in F.

A_v = voltage gain.

C_{bc} = internal capacitance of the BJT from base to collector in F.

ii. Frequency response of C_o :

$$\begin{aligned} f_{H_o} &= \frac{1}{2\pi R_{Th_o} C_o} \\ R_{Th_o} &= R_C \parallel R_L \parallel r_o \\ C_o &= C_{W_o} + C_{ce} + C_{M_o} \\ C_o &= C_{W_o} + C_{ce} + (1 - 1/A_v)C_{bc} \end{aligned}$$

Where:

C_{W_o} = output wiring capacitance in F.

C_{ce} = internal capacitance of the BJT from collector to emitter in F.

C_{M_o} = output Miller effect capacitance in F.

A_v = voltage gain.

After calculating these frequencies, we can get the values for the low band and high band frequency. However, to find the gain of this amplifier we can use:

The total gain of the circuit:

$$A_{v_s} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s}$$

**The gain of the amplifier:
(Without the effect of R_s).**

$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel R_L}{r_e}$$

**The resulted gain:
(After adding R_s).**

$$A_{v_{mid}} = \frac{V_o}{V_s} = \frac{R_i}{R_i + R_s}$$

3. Implementation & Analysis

This section will contain the simulation of the circuit with its bode plot and characteristics values of f_L and f_H . In addition, the analysis of the frequency response and a comparison between the practical and theoretical values.

❖ Implementation

I will use the previous circuit discussed in **Figure 2** with the parameters shown in the next Figure:

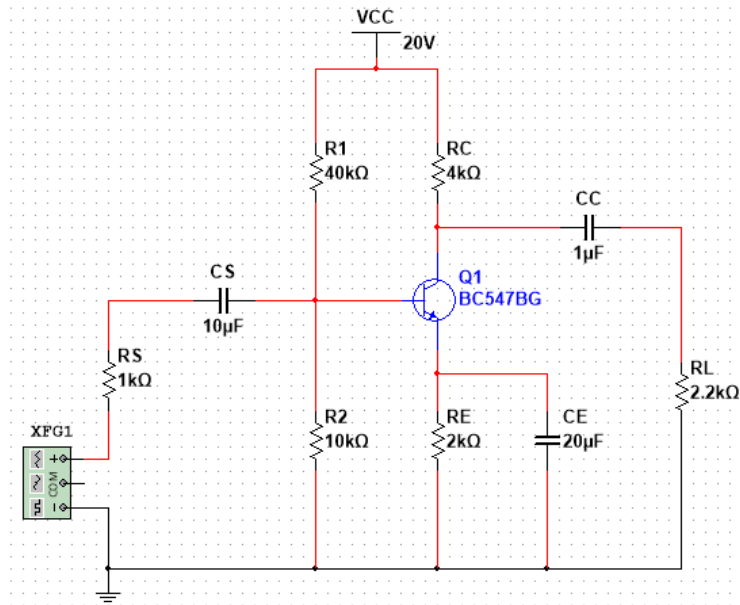


Figure 4 – S

So, now we can calculate the theoretical values to compare them later with the practical values.

1- Low Frequency Response:

A- Response of Capacitor S:

Using the following equations: (with **beta = 120** from **Figure 6** of the datasheet of BC547BG)

$$f_{L_s} = \frac{1}{2\pi(R_i + R_s)C_s} \quad R_i = R_1 \parallel R_2 \parallel \beta r_e$$

We get:

$$V_B \cong \frac{R_2 V_{CC}}{R_2 + R_1} = \frac{10 \text{ k}\Omega (20 \text{ V})}{10 \text{ k}\Omega + 40 \text{ k}\Omega} = \frac{200 \text{ V}}{50} = 4 \text{ V} \quad \text{from (DC analysis)}$$

$$I_E = \frac{V_E}{R_E} = \frac{4 \text{ V} - 0.7 \text{ V}}{2 \text{ k}\Omega} = \frac{3.3 \text{ V}}{2 \text{ k}\Omega} = 1.65 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{1.65 \text{ mA}} \cong 15.76 \text{ }\Omega, \quad \beta r_e = 120 * 15.76 = 1.891 \text{ k}\Omega$$

$$R_i = R_1 \parallel R_2 \parallel \beta r_e = 10\text{k} // 40\text{k} // 1.891\text{k} = 1.529 \text{ k}\Omega$$

$$f_{L_s} = \frac{1}{2\pi(1.529\text{k} + 1\text{k})10\mu} = 6.29 \text{ Hz}$$

B- Response of Capacitor C:

Using the following equations:

$$f_{LC} = \frac{1}{2\pi(R_o + R_L)C_C} \quad \text{with } R_o = R_C \parallel r_o \cong R_C$$

Because $r_o = 1 \text{ G}\Omega \cong \infty$

$$f_{LC} = \frac{1}{2\pi(R_o + R_L)C_C} = \frac{1}{2\pi(4k + 2.2k)1\mu} = \mathbf{25.67 \text{ Hz}}$$

C- Response of Capacitor E:

$$f_{LE} = \frac{1}{2\pi R_e C_E}, \quad R_e = R_E \parallel \left(\frac{R'_s}{\beta} + r_e \right) \text{ and } R'_s = R_s \parallel R_1 \parallel R_2$$

$R'_s = 889 \Omega$, $R_e = 24 \Omega$

$$f_{LE} = \frac{1}{2\pi(24)20\mu} = \mathbf{331.57 \text{ Hz}}$$

- $f_L = \max(f_{LS}, f_{LC}, f_{LE}) = f_{LE} = \mathbf{331.57 \text{ Hz}}$

2- High Frequency Response:

A- Response of C_i:

Using the following equations: ($C_i = 10 \text{ pF}$, from the datasheet)

$$f_{Hi} = \frac{1}{2\pi R_{Thi} C_i} \quad R_{Thi} = R_s \parallel R_1 \parallel R_2 \parallel \beta r_e$$

$$C_i = C_{Wi} + C_{be} + C_{Mi} = C_{Wi} + C_{be} + (1 - A_v)C_{bc}$$

$$R_{Thi} = 605 \Omega, C_i = 10 \text{ pF}, f_{Hi} = \frac{1}{2\pi(605)10p} = \mathbf{26.31 \text{ MHz}}$$

B- Response of C_o:

Using the following equations: ($C_o = 1.7 \text{ pF}$, from the datasheet)

$$f_{Ho} = \frac{1}{2\pi R_{Tho} C_o} \quad R_{Tho} = R_C \parallel R_L \parallel r_o$$

$$C_o = C_{Wo} + C_{ce} + C_{Mo}$$

$$R_{Tho} = 1419 \Omega \text{ (taking } r_o = 1 \text{ G}\Omega \cong \infty), C_o = 1.7 \text{ pF}, f_{Ho} = \frac{1}{2\pi(1419)1.7p} = \mathbf{65.98 \text{ MHz}}$$

- $f_H = \min(f_{Hi}, f_{Ho}) = f_{Hi} = \mathbf{26.31 \text{ MHz}}$

3- The Voltage Gain:

$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel R_L}{r_e} = \frac{-1419}{15.76} = -90.04$$

$$A_{v_{mid}} = \frac{V_b}{V_s} = \frac{R_i}{R_i + R_s} = \frac{1529}{1529 + 1000} = 0.60$$

$$A_{v_s} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_b}{V_s} = -90.04 \cdot 0.60 = -54.02$$

- $dB \text{ Gain} = 20 \log(54.02) = 34.65 \text{ dB}$

Now, after calculating the theoretical values, using Bode Plotter, we can find the practical value from the bode plot of the circuit:

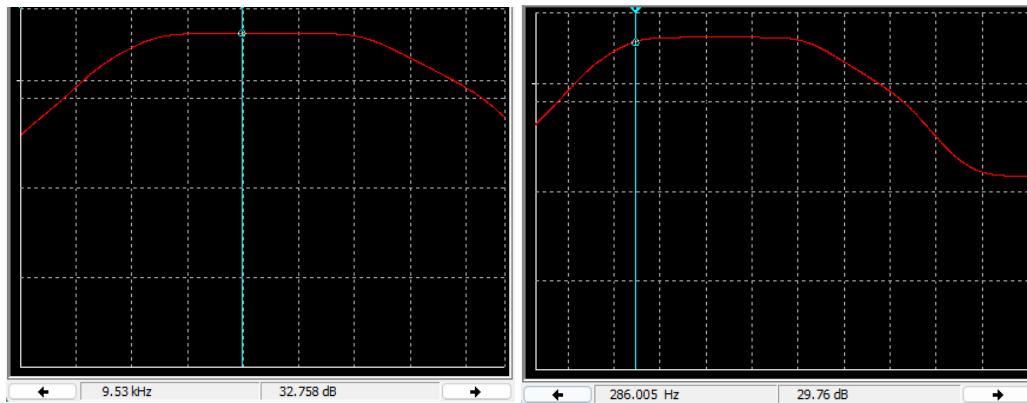


Figure 5 – a

Figure 5 – b

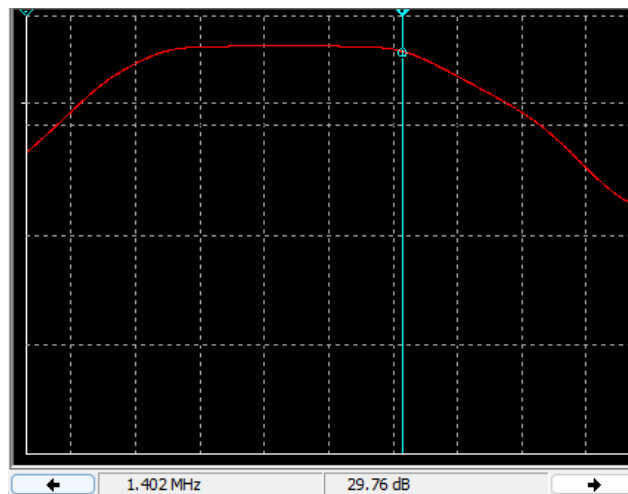


Figure 5 – c

Figure 5 – Bode Plot

Figure 5 – a: represents the overall bode plot of this BPF.

Figure 5 – b: represents the LPF at practical cutoff frequency of 286.01 Hz, by taking -3 dB from the mid band gain.

Figure 5 – c: represents the HPF at practical cutoff frequency of 1.40 MHz, by taking -3 dB from the mid band gain.

Finally, here is the phase plot:

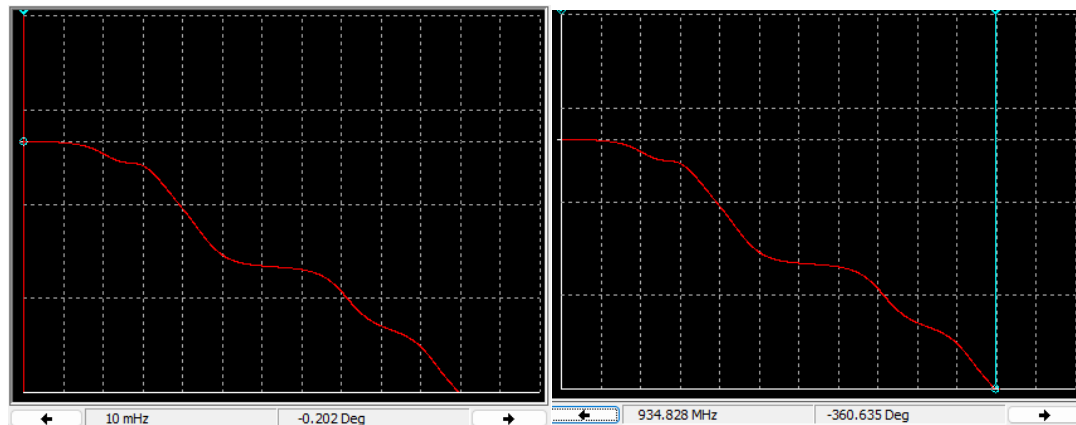


Figure 6 – Phase Bode Plot

❖ Analysis

In this section I will discuss the previous results using the following table:

Parameter	Theoretical	Particle	Error
Low Frequency	331.57 Hz	286.01 Hz	13.74%
High Frequency	26.31 MHz	1.40 MHz	High
Gain	34.65 dB	32.76 dB	5.45%

It is well known that frequency analysis differs excessively between practice and theory. However, here are some reasons of this percentages:

- 1- There could be some little noise.
- 2- There were a lot of approximations in the calculations.
- 3- These errors are for the values that are found and calculated on a logarithmic scale, so it is possible to have some extreme percentages for error.
- 4- For the high frequency calculation: the capacitance values of the wiring were neglected because we do not have these values, and it is known that when we have such a situation, we try to find the value of the high cutoff frequency only practically (because each type of wiring has its own internal capacitance value). "In the high-frequency region, the capacitive elements of importance are the interelectrode (between-terminals) capacitances internal to the active device and the wiring capacitance between leads of the network". (Boylestad, 2012, p. 574)

4. Conclusion

At the end, I have constructed and analyzed an active BPF circuit using voltage divider BJT network. In this project, I have applied an abundance amount of knowledge that I have learned in Electronics 2 course. Finally, the analysis shows that this application of BJT is very useful and has its own benefits & negatives.

5. References

Alldatasheet.com. (n.d.). *BC546 Datasheet(PDF) - on semiconductor*.

ALLDATASHEET.COM - Electronic Parts Datasheet Search. Retrieved December 15, 2022, from <https://www.alldatasheet.com/datasheet-pdf/pdf/11550/ONSEMI/BC546.html>

Boylestad, Robert L., and Louis Nashelsky. *Electronic devices and circuit theory*. Prentice Hall, 2012.

Sedra, Adel S., et al. *Microelectronic circuits*. Vol. 4. New York: Oxford university press, 2004.