



# Electronics 2

## Active BPF using BJT

Marwan Bitar / 4110259

# TABLE OF CONTENT

01

Introduction

02

Theory

03

Configuration

04

Implementation

05


Analysis

06

Conclusion
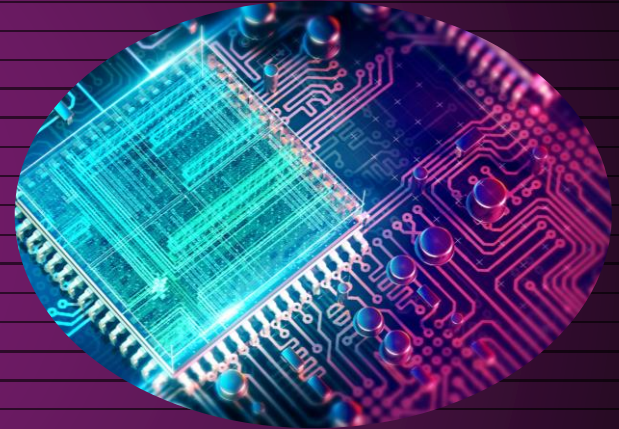
# INTRODUCTION


- The Significance
- Active Filter
- BPF
- BJT




# Theory

$$\text{bandwidth (BW)} = f_H - f_L$$

$$f = \frac{1}{2\pi RC}$$

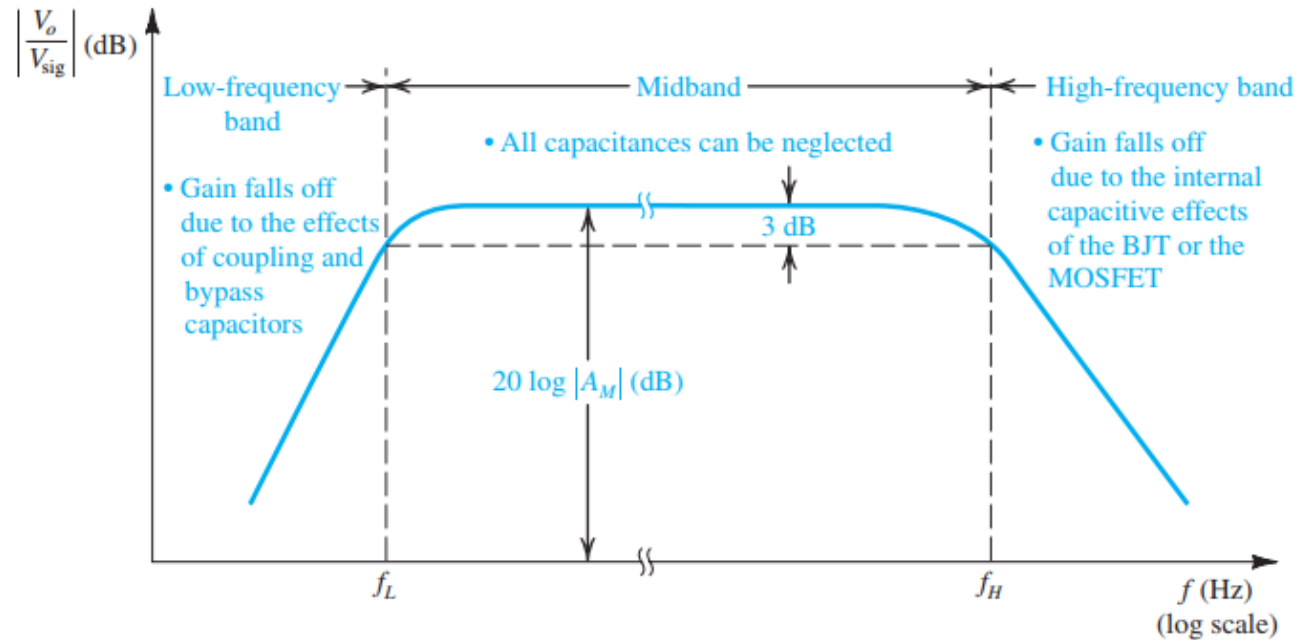

# Configuration

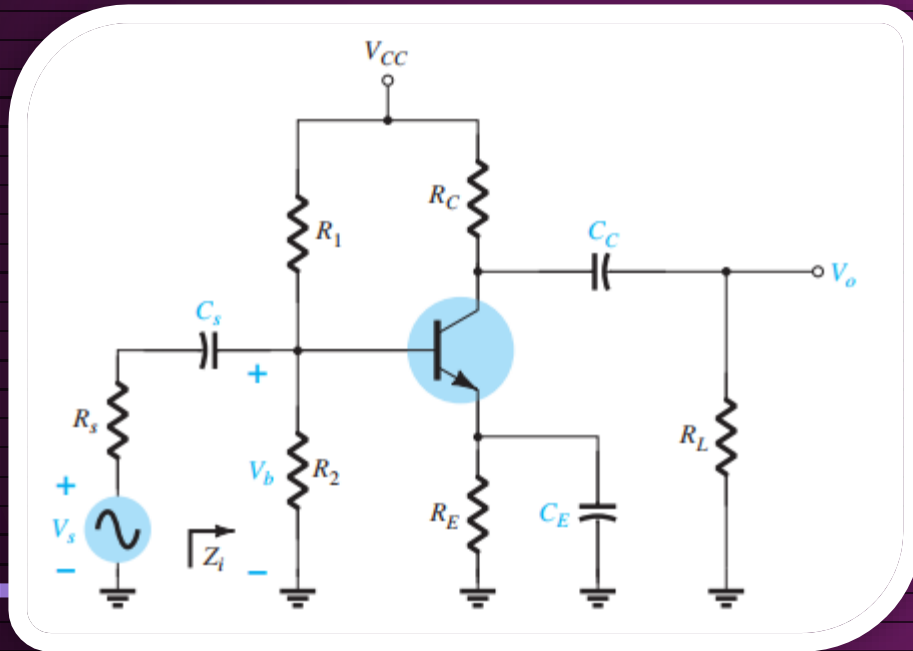

Voltage divider  
common-  
emitter BJT  
circuit

# Low Frequency Response

## Capacitor S

$$f_{L_s} = \frac{1}{2\pi(R_i + R_s)C_s}$$

$$R_i = R_1 \parallel R_2 \parallel \beta r_e$$

## Capacitor C

$$f_{L_c} = \frac{1}{2\pi(R_o + R_L)C_C}$$

$$R_o = R_C \parallel r_o$$

## Capacitor E


$$f_{L_E} = \frac{1}{2\pi R_e C_E}$$

$$R_e = R_E \parallel \left( \frac{R'_s}{\beta} + r_e \right)$$

$$\text{and } R'_s = R_s \parallel R_1 \parallel R_2$$

$$f_L = \max(f_s, f_C, f_E)$$
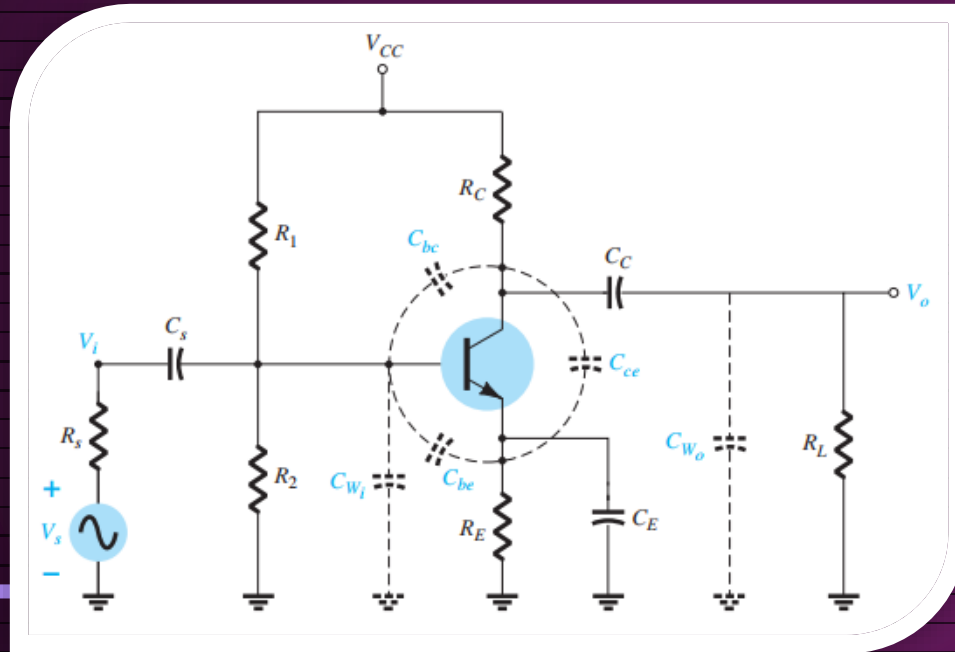
# Configuration of High Frequency Response



Same BJT  
configuration  
with the effect  
of the output  
capacitance

# High Frequency Response

$$f_{H_i} = \frac{1}{2\pi R_{Th_i} C_i}$$

$$R_{Th_i} = R_s \parallel R_1 \parallel R_2 \parallel \beta r_e$$

$$C_i = C_{W_i} + C_{be} + C_{M_i} = C_{W_i} + C_{be} + (1 - A_v)C_{bc}$$

Capacitance  $C_i$

$$f_H = \min(f_{H_i}, f_{H_o})$$

Capacitance  $C_o$

$$f_{H_o} = \frac{1}{2\pi R_{Th_o} C_o}$$

$$R_{Th_o} = R_C \parallel R_L \parallel r_o$$

$$C_o = C_{W_o} + C_{ce} + C_{M_o}$$

$$C_o = C_{W_o} + C_{ce} + (1 - 1/A_v)C_{bc}$$



# The Gain

❑ The total gain:

$$A_{v_s} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_i}{V_s}$$


❑ The gain of the amplifier  
(without the effect of  $R_s$ )

$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel R_L}{r_e}$$

❑ The resulted gain:  
(after adding  $R_s$ )

$$A_{v_{mid}} = \frac{V_o}{V_s} = \frac{R_i}{R_i + R_s}$$

# Implementation

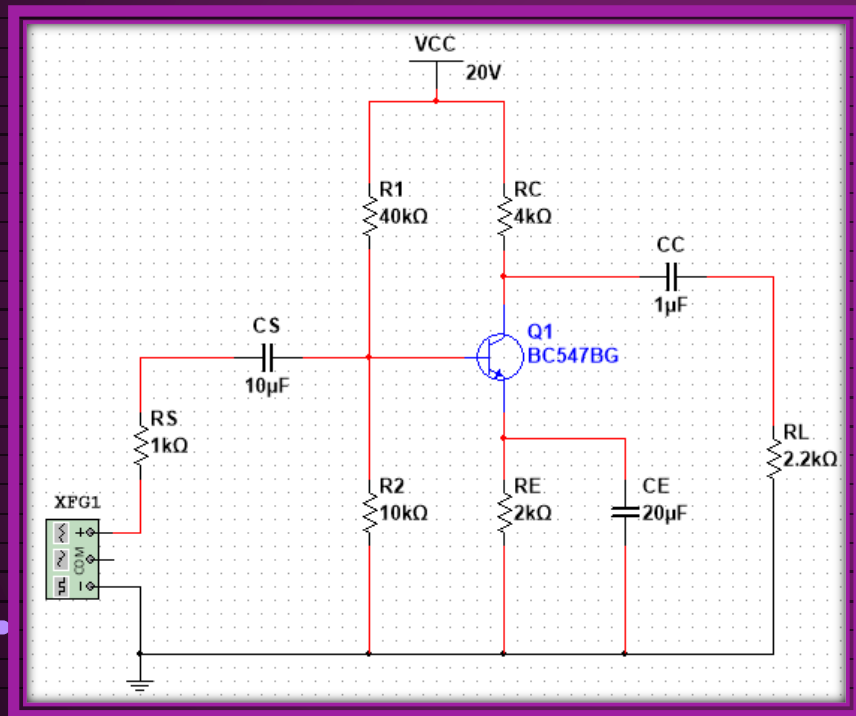

Circuit  
Simulation

# Low Frequency Response

$$f_{L_s} = \frac{1}{2\pi(R_i + R_s)C_s}$$

$$R_i = R_1 \parallel R_2 \parallel \beta r_e$$

Capacitor S

$$V_B \cong \frac{R_2 V_{CC}}{R_2 + R_1} = \frac{10 \text{ k}\Omega (20 \text{ V})}{10 \text{ k}\Omega + 40 \text{ k}\Omega} = \frac{200 \text{ V}}{50} = 4 \text{ V} \quad \text{from (DC analysis)}$$

$$I_E = \frac{V_E}{R_E} = \frac{4 \text{ V} - 0.7 \text{ V}}{2 \text{ k}\Omega} = \frac{3.3 \text{ V}}{2 \text{ k}\Omega} = 1.65 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{1.65 \text{ mA}} \cong 15.76 \text{ }\Omega, \quad \beta r_e = 120 * 15.76 = 1.891 \text{ k}\Omega$$

$$R_i = R_1 \parallel R_2 \parallel \beta r_e = 10 \text{ k}\Omega / 40 \text{ k}\Omega / 1.891 \text{ k}\Omega = 1.529 \text{ k}\Omega$$

$$f_{L_s} = \frac{1}{2\pi(1.529 \text{ k} + 1 \text{ k})10 \mu} = 6.29 \text{ Hz}$$

# Low Frequency Response



$$f_{L_C} = \frac{1}{2\pi(R_o + R_L)C_C}$$

$$R_o = R_C \parallel r_o$$

Capacitor C

Using the following equations:

$$f_{L_C} = \frac{1}{2\pi(R_o + R_L)C_C} \quad \text{with} \quad R_o = R_C \parallel r_o \cong R_C$$

Because  $r_o = 1 \text{ G}\Omega \cong \infty$

$$f_{L_C} = \frac{1}{2\pi(R_o + R_L)C_C} = \frac{1}{2\pi(4k + 2.2k)1\mu} = 25.67 \text{ Hz}$$

# Low Frequency Response

$$f_{L_E} = \frac{1}{2\pi R_e C_E}$$

$$R_e = R_E \parallel \left( \frac{R'_s}{\beta} + r_e \right)$$

$$\text{and } R'_s = R_s \parallel R_1 \parallel R_2$$

$$f_{L_E} = \frac{1}{2\pi R_e C_E}, \quad R_e = R_E \parallel \left( \frac{R'_s}{\beta} + r_e \right) \text{ and } R'_s = R_s \parallel R_1 \parallel R_2$$

$$R_s' = 889 \, \Omega, R_e = 24 \, \Omega$$

$$f_{L_E} = \frac{1}{2\pi(24)20\mu} = \mathbf{331.57 \, Hz}$$

Capacitor E

$$f_L = \max(f_s, f_C, f_E) = 331.57 \, \text{Hz}$$

# High Frequency Response

$$f_{H_i} = \frac{1}{2\pi R_{Th_i} C_i}$$

$$R_{Th_i} = R_s \parallel R_1 \parallel R_2 \parallel \beta r_e$$

$$C_i = C_{W_i} + C_{be} + C_{M_i} = C_{W_i} + C_{be} + (1 - A_v)C_{bc}$$

Capacitance  $C_i$

$$R_{Th_i} = 605 \, \Omega, C_i = 10 \, \text{pF}, f_{H_i} = \frac{1}{2\pi(605)10\text{p}} = \mathbf{26.31 \, MHz}$$

# High Frequency Response

$$f_{H_o} = \frac{1}{2\pi R_{Th_o} C_o}$$

$$R_{Th_o} = R_C \parallel R_L \parallel r_o$$

$$C_o = C_{W_o} + C_{ce} + C_{M_o}$$

$$C_o = C_{W_o} + C_{ce} + (1 - 1/A_v)C_{bc}$$

Capacitance  $C_o$

$$R_{Th_o} = 1419 \, \Omega \text{ (taking } r_o = 1 \, \text{G}\Omega \cong \infty), C_o = 1.7 \, \text{pF}, f_{H_o} = \frac{1}{2\pi(1419)1.7p} = 65.98 \, \text{MHz}$$

$$f_H = \min(f_{H_i}, f_{H_o}) = 26.31 \, \text{MHz}$$

# The Gain



$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel R_L}{r_e} = \frac{-1419}{15.76} = -90.04$$

$$A_{v_{\text{mid}}} = \frac{V_b}{V_s} = \frac{R_i}{R_i + R_s} = \frac{1529}{1529 + 1000} = 0.60$$


$$A_{v_s} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \cdot \frac{V_b}{V_s} = -90.04 * 0.60 = -54.02$$
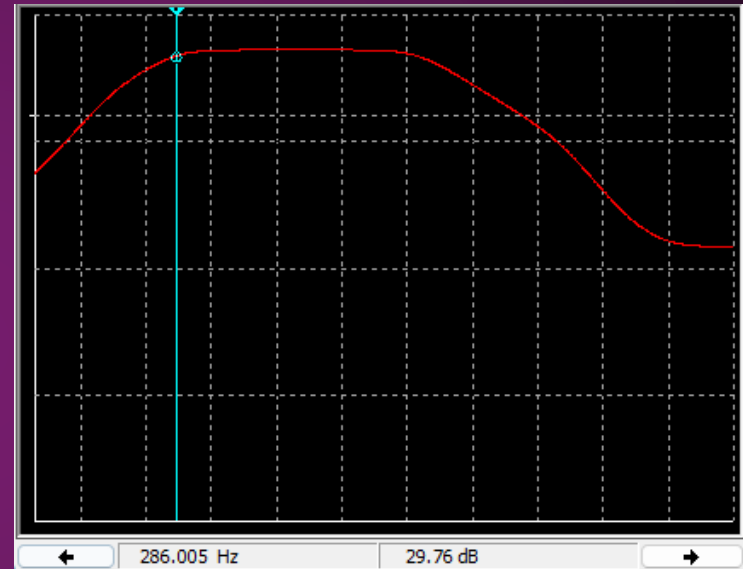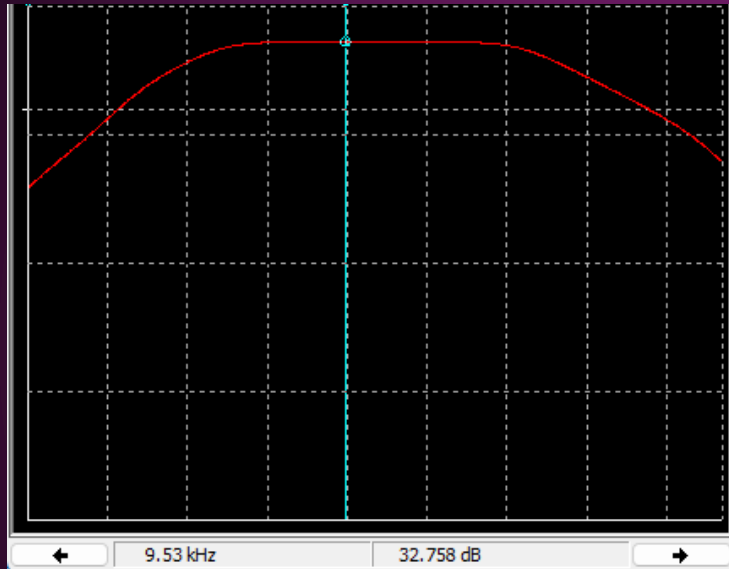
$$\begin{aligned} \text{dB Gain} \\ &= 20 \log(54.02) \\ &= 34.65 \text{ dB} \end{aligned}$$






**Bode Plot – Magnitude**

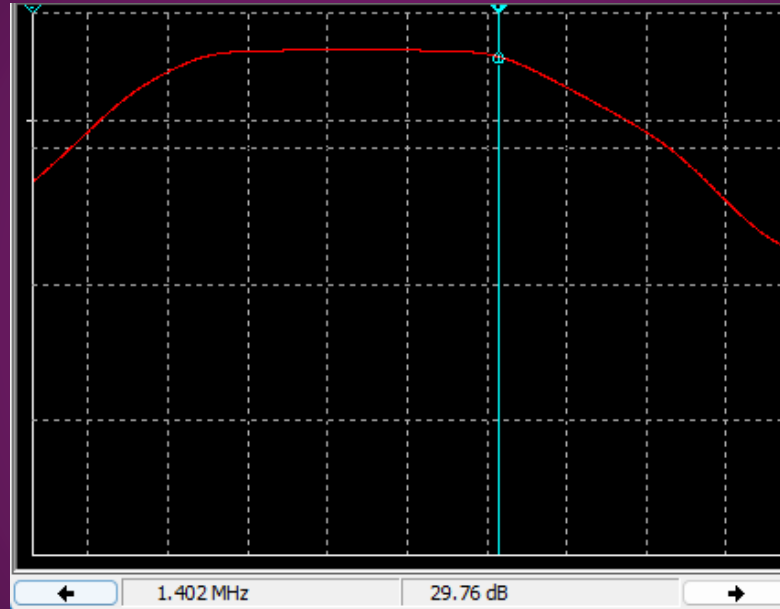

**Bode Plot – Magnitude**

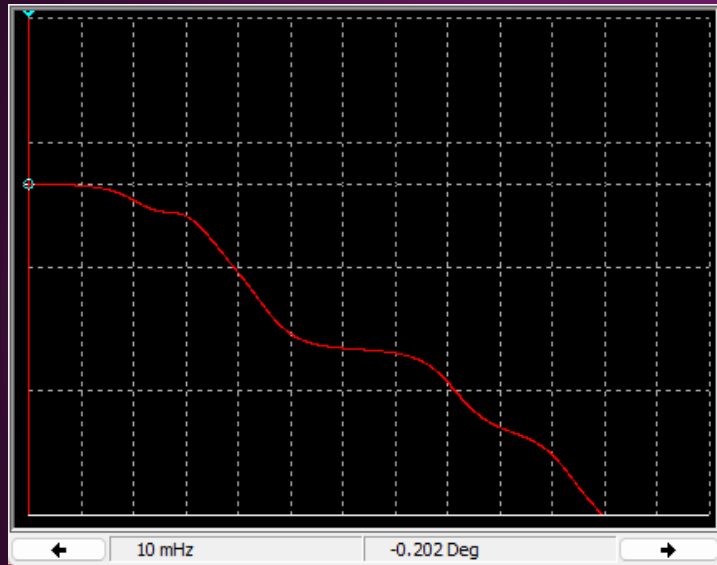

## Bode Plot – Phase


# Analysis

- Noise
- Approximations in the calculations
- Values are found and calculated on a logarithmic scale

Parameter	Theoretical	Particle	Error
Low Frequency	331.57 Hz	286.01 Hz	13.74%
High Frequency	26.31 MHz	1.40 MHz	High
Gain	34.65 dB	32.76 dB	5.45%
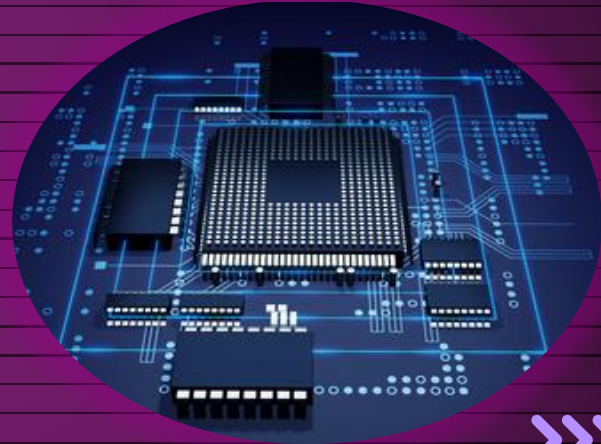
# Conclusion

- **Circuit Construction**
- **Analysis**
- **Course Knowledge**



**Thank you!**

**Questions?**